



ELEC373
Digital Systems Design
Assignment 3
MIP Processor

Junhao Zhang
201377244

20 March 2020

Declaration

I confirm that I have read and understood the University's definitions of plagiarism and collusion from the Code of Practice on Assessment. I confirm that I have neither committed plagiarism in the completion of this work nor have I colluded with any other party in the preparation and production of this work. The work presented here is my own and in my own words except where I have clearly indicated and acknowledged that I have quoted or used figures from published or unpublished sources (including the web). I understand the consequences of engaging in plagiarism and collusion as described in the Code of Practice on Assessment (Appendix L).

1 Contents

2	Introduction	3
3	Part A: Displaying ID on the 7-segment LED	3
3.1	Assembly Language Code.....	3
3.2	ModelSim Result.....	4
3.3	A Photograph of the 7-segment Displays.....	5
4	Part B: Implementation of Additional Instructions.....	6
4.1	Modified Modules	6
4.1.1	Byte Address Decider	7
4.1.2	Mips.....	8
4.1.3	Main Decoder	9
4.1.4	ALU Decoder.....	10
4.1.5	ALU	11
4.1.6	Datapath.....	12
4.1.7	Load Byte	15
4.2	NOR.....	16
4.2.1	Assembly Language Code	16
4.2.2	ModelSim Result	16
4.3	ANDI	17
4.3.1	Assembly Language Code	17
4.3.2	ModelSim Result	17
4.4	LBU	17
4.4.1	Assembly Language Code	17
4.4.2	Additional Pathways Diagram.....	18

2 Introduction

In this assignment, there are two parts including developing an assembly language code to display the lower 8 digits of student ID number and implementing three additional instructions by modifying the Verilog codes. Some assembly programs are developed in order to prove that the instructions are working properly. The simulations result generated from the ModelSim demonstrate that the desired function can be achieved.

3 Part A: Displaying ID on the 7-segment LED

3.1 Assembly Language Code

```
# number 0
lui $s0, 0x0000
addiu $s0, $s0, 0x0040
# number 1
lui $s1, 0x0000
addiu $s1, $s1, 0x0079
# number 3
lui $s2, 0x0000
addiu $s2, $s2, 0x0030
# number 7
lui $s3, 0x0000
addiu $s3, $s3, 0x0078
# number 7
lui $s4, 0x0000
addiu $s4, $s4, 0x0078
# number 2
lui $s5, 0x0000
addiu $s5, $s5, 0x0024
# number 4
lui $s6, 0x0000
addiu $s6, $s6, 0x0019
# number 4
lui $s7, 0x0000
addiu $s7, $s7, 0x0019

# 7-segment HEX7
lui $t0, 0xffff
addiu $t0, $t0, 0x202C
# 7-segment HEX6
lui $t1, 0xffff
addiu $t1, $t1, 0x2028
# 7-segment HEX5
lui $t2, 0xffff
addiu $t2, $t2, 0x2024
# 7-segment HEX4
```

 



Figure 2: ModelSim Simulation Result

As demonstrated in Figure 1 and Figure 2, the simulation result shows that the 8 numbers are in succession stored into the memories with the addresses from 0xFFFF2010 to 0xFFFF202C when each sw instruction is executed. The hexadecimal numbers indicates the LEDs on the 7-segment display and the numbers are respectively 0, 1, 3, 7, 7, 2, 4, 4 displayed on the 7-segment.

3.3 A Photograph of the 7-segment Displays

 


Figure 3: ID Displayed on the 7-segment

4 Part B: Implementation of Additional Instructions

4.1 Modified Modules

In the following sections, the modified Verilog code for the modules are highlighted with red underline. Also included are some extra module added into the Verilog code.

4.1.1 Byte Address Decider

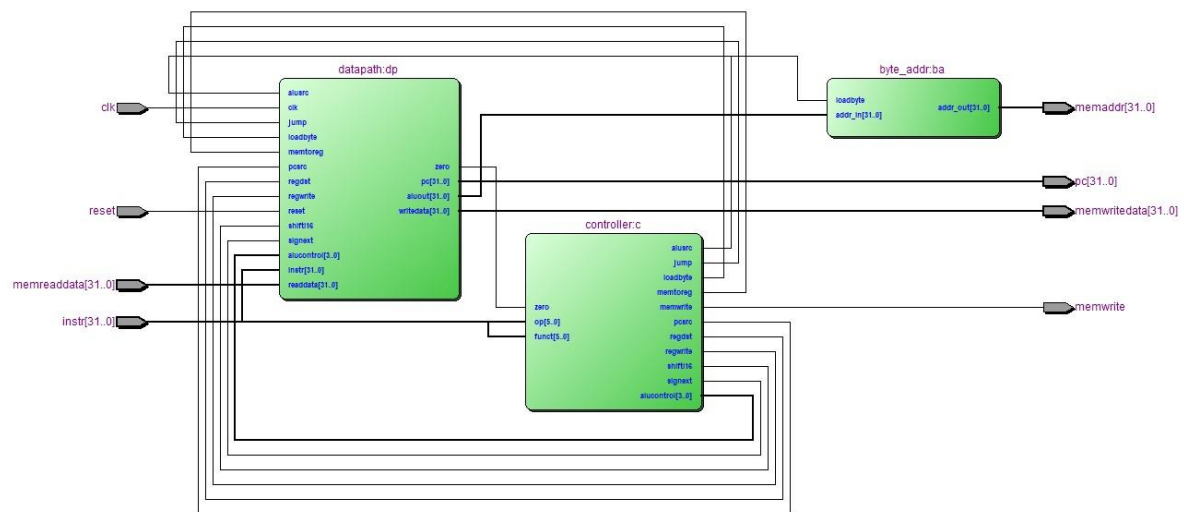


Figure 4: Modified Block Diagram

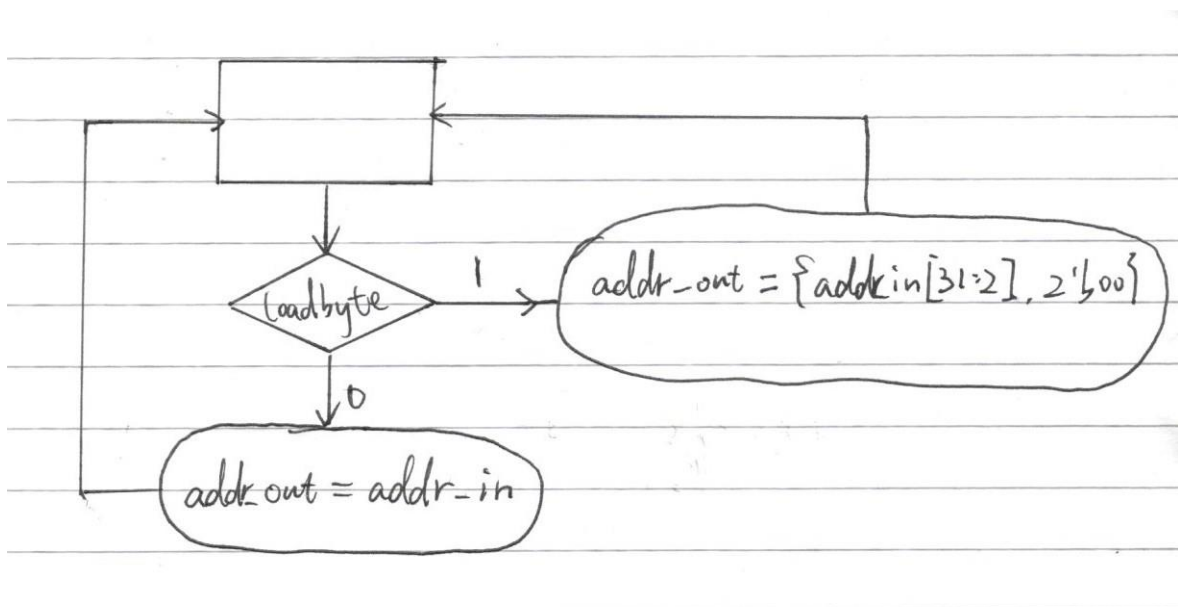


Figure 5: ASM

```

module byte_addr( input    [31:0] addr_in,
                  input      loadbyte,
                  output reg [31:0] addr_out);

always @(*)
begin
    if(loadbyte)
        addr_out <= {addr_in[31:2], 2'b00};
    else
        addr_out <= addr_in;
end

```

```
endmodule
```

This module is connected between the aluout signal from the data path and the memaddr signal of the memory. It determines whether a full 32 bit data should be transmitted to the memory or a 32 bit data with the least two significant bits replaced by two bits of zeros. This is depending on the loadbyte signal which indicates whether the instruction is requiring to load a byte from the memory.

4.1.2 Mips

```
module mips(input      clk, reset,
            output [31:0] pc,
            input  [31:0] instr,
            output      memwrite,
            output [31:0] memaddr,
            output [31:0] memwritedata,
            input  [31:0] memreaddata);

    wire      signext, shiftl16, memtoreg, branch;
    wire      pcsrc, zero;
    wire      alusrc, regdst, regwrite, jump;
    wire      loadbyte;
    wire [3:0] alucontrol;
    wire [31:0] aluout;

    // Instantiate Controller
    controller c(.op      (instr[31:26]),
                 .funct    (instr[5:0]),
                 .zero     (zero),
                 .signext  (signext),
                 .shiftl16 (shiftl16),
                 .memtoreg (memtoreg),
                 .memwrite (memwrite),
                 .pcsrc    (pcsrc),
                 .alusrc   (alusrc),
                 .regdst   (regdst),
                 .regwrite (regwrite),
                 .loadbyte (loadbyte),
                 .jump     (jump),
                 .alucontrol (alucontrol));

    // Instantiate Datapath
    datapath dp( .clk      (clk),
                 .reset    (reset),
                 .signext  (signext),
                 .shiftl16 (shiftl16),
```



```

        .memtoreg    (memtoreg),
        .pcsrc       (pcsrc),
        .alusrc      (alusrc),
        .regdst       (regdst),
        .regwrite     (regwrite),
        .loadbyte     (loadbyte),
        .jump         (jump),
        .alucontrol   (alucontrol),
        .zero         (zero),
        .pc           (pc),
        .instr        (instr),
        .aluout        (aluout),
        .writedata     (memwritedata),
        .readdata      (memreaddata));

    byte_addr ba(.addr in(aluout),
               .loadbyte(loadbyte),
               .addr out(memaddr));

endmodule

```

For the MIPS module, an additional module `byte_addr` is added in order to select the proper memory address from the `aluout`. Because the LBU instruction requires a different memory address which is modified by replacing the last two bits with zeros, the module can output different memory address format depending on the `loadbyte` signal.

4.1.3 Main Decoder

```

module maindec(input  [5:0] op,
               output  signext,
               output  shiftl16,
               output  memtoreg, memwrite,
               output  branch, alusrc,
               output  regdst, regwrite,
               output  loadbyte,
               output  jump,
               output [2:0] aluop);

    reg [13:0] controls;

    assign {signext, shiftl16, regwrite, regdst,
           alusrc, branch, memwrite,
           memtoreg, loadbyte, jump, aluop} = controls;

    always @(*)
        case(op)
            6'b000000: controls <= 13'b0011000000100; // Rtype

```

```

        6'b100011: controls <= 13'b10101001000000; // LW
        6'b100100: controls <= 13'b10101001100000; // LBU
        6'b101011: controls <= 13'b10001010000000; // SW
        6'b000100: controls <= 13'b10000100000001; // BEQ
        6'b001000,
        6'b001001: controls <= 13'b10101000000000; // ADDI, ADDIU: only difference
is exception
        6'b001101: controls <= 13'b00101000000010; // ORI
        6'b001100: controls <= 13'b00101000000011; // ANDI
        6'b001111: controls <= 13'b01101000000000; // LUI
        6'b000010: controls <= 13'b00000000001000; // J
        default: controls <= 13'bxxxxxxxxxxxxxx; // ???
    endcase
endmodule

```

In order to add three additional instructions, the main decoder should be modified to have the corresponding control signals for those instructions. Additionally, a loadbyte signal is added into the set of the control signals and it only becomes 1 when the opcode is detected as the LBU instruction.

4.1.4 ALU Decoder

```

module aludec(input [5:0] funct,
               input [2:0] aluop,
               output reg [3:0] alucontrol);

    always @(*)
        case(aluop)
            3'b000: alucontrol <= 4'b0010; // add
            3'b001: alucontrol <= 4'b0110; // sub
            3'b010: alucontrol <= 4'b0001; // or
            3'b011: alucontrol <= 4'b0000; // and
            3'b100: // RTYPE
                case(funct)
                    6'b100000,
                    6'b100001: alucontrol <= 4'b0010; // ADD, ADDU: only difference
is exception
                    6'b100010,
                    6'b100011: alucontrol <= 4'b0110; // SUB, SUBU: only difference
is exception
                    6'b100100: alucontrol <= 4'b0000; // AND
                    6'b100101: alucontrol <= 4'b0001; // OR
                    6'b101010: alucontrol <= 4'b0111; // SLT
                    6'b100111: alucontrol <= 4'b1100; // NOR
                    default: alucontrol <= 4'bxxxx; // ???
                endcase
        endcase

```

```

        default: alucontrol <= 4'bxxxx; // ???
    endcase
endmodule

```

In order to implement the NOR instruction, an additional function code NOR is implement into the R-type instruction. This generates a unique alucontrol signal which lead the ALU to perform a NOR operation.

4.1.5 ALU

```

module alu(input [31:0] a, b,
           input [3:0] alucont,
           output reg [31:0] result,
           output zero);

    wire [31:0] a2, b2, sum, slt;

    assign a2 = alucont[3] ? ~a:a;
    assign b2 = alucont[2] ? ~b:b;
    assign sum = a2 + b2 + alucont[3] + alucont[2];
    assign slt = sum[31];

    always@(*)
        case(alucont[1:0])
            2'b00: result <= a2 & b2;
            2'b01: result <= a2 | b2;
            2'b10: result <= sum;
            2'b11: result <= slt;
        endcase

    assign zero = (result == 32'b0);

endmodule

```

As mentioned in the previous section, the alucontrol signal for the NOR instruction generated from the ALU decoder is 1100. Therefore, it leads the ALU to perform a AND operation of the two input but with a NOT in front of them. By the De Morgan's law, NOT a AND NOT b equals a NOR b, and this renders the ALU perform the NOR operation equivalently. For the ANDI instruction, the ALU just AND the two inputs without a NOT in front of them.

4.1.6 Datapath

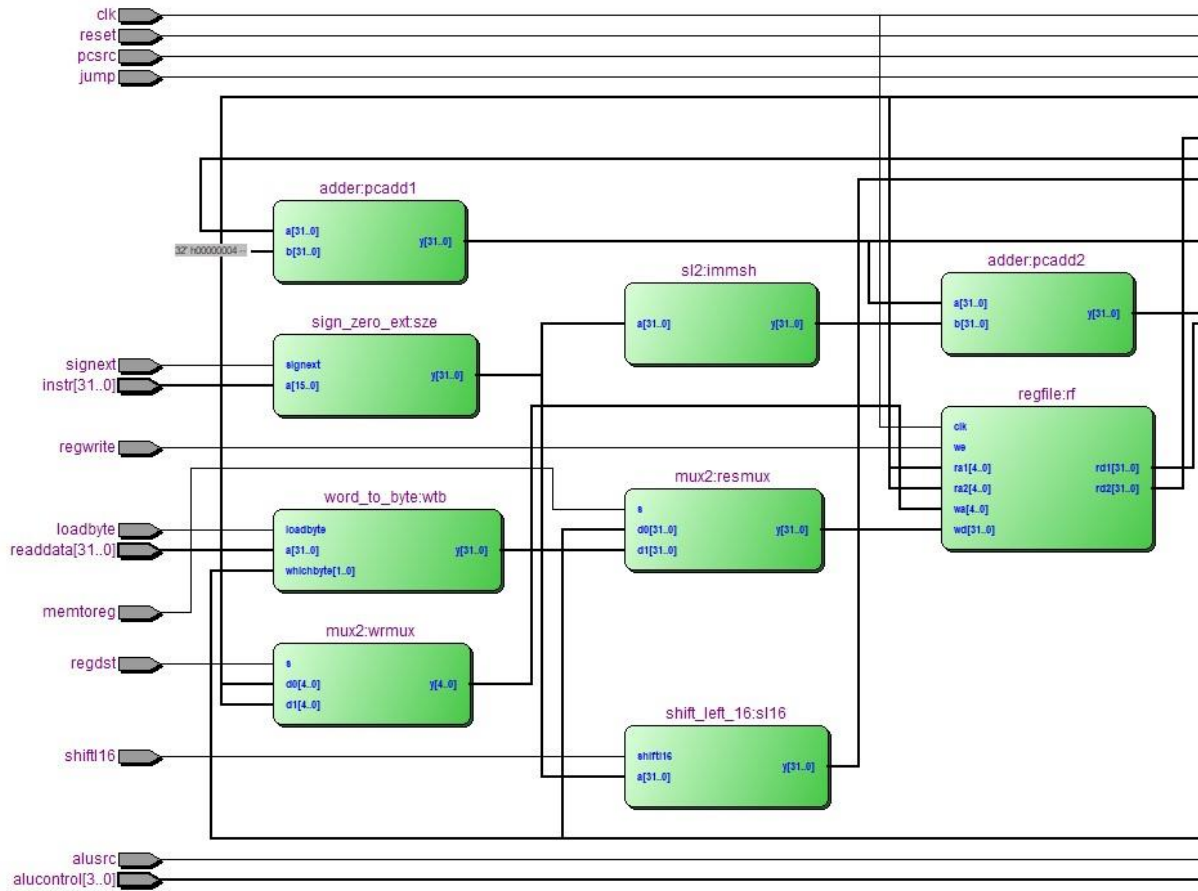


Figure 6: Modified Block Diagram

```

module datapath(input      clk, reset,
                input      signext,
                input      shiftl16,
                input      memtoreg, pcsrc,
                input      alusrc, regdst,
                input      regwrite, jump,
                input      loadbyte,
                input  [3:0] alucontrol,
                output      zero,
                output  [31:0] pc,
                input  [31:0] instr,
                output  [31:0] aluout, writedata,
                input  [31:0] readdata);

wire [4:0] writereg;
wire [31:0] pcnext, pcnextbr, pcplus4, pcbranch;
wire [31:0] signimm, signimmsh, shiftedimm;
wire [31:0] srca, srcb;
wire [31:0] result;

```

```

wire [31:0] memdata;
wire        shift;

// next PC logic
flopr #(32) pcreg (.clk  (clk),
                  .reset (reset),
                  .d     (pcnext),
                  .q     (pc));

adder      pcadd1 (.a (pc),
                  .b (32'b100),
                  .y (pcplus4));

sl2        immsh (.a (signimm),
                  .y (signimmsh));

adder      pcadd2 (.a (pcplus4),
                  .b (signimmsh),
                  .y (pcbranch));

mux2 #(32) pcbrmux(.d0 (pcplus4),
                  .d1 (pcbranch),
                  .s  (pcsrc),
                  .y  (pcnextbr));

mux2 #(32) pcmux (.d0 (pcnextbr),
                  .d1 ({pcplus4[31:28], instr[25:0], 2'b00}),
                  .s  (jump),
                  .y  (pcnext));

// register file logic
regfile   rf(.clk  (clk),
             .we    (regwrite),
             .ra1    (instr[25:21]),
             .ra2    (instr[20:16]),
             .wa     (writereg),
             .wd     (result),
             .rd1    (srca),
             .rd2    (writedata));

mux2 #(5)  wrmux(.d0 (instr[20:16]),
                 .d1 (instr[15:11]),
                 .s  (regdst),
                 .y  (writereg));

mux2 #(32) resmux(.d0 (aluout),
                  .d1 (memdata),
                  .s  (memtoreg),

```

```

        .y (result));

sign_zero_ext  sze(.a      (instr[15:0]),
                  .signext (signext),
                  .y       (signimm[31:0]));

word_to_byte  wtb(.a      (readdata),
                  .loadbyte (loadbyte),
                  .whichbyte (aluout[1:0]),
                  .y       (memdata));

shift_left_16 sl16(.a      (signimm[31:0]),
                  .shiftl16 (shiftl16),
                  .y       (shiftedimm[31:0]));

// ALU logic
mux2 #(32)  srcbmux(.d0 (writedata),
                  .d1 (shiftedimm[31:0]),
                  .s  (alusrc),
                  .y  (srcb));

alu        alu( .a      (srca),
               .b      (srcb),
               .alucont (alucontrol),
               .result  (aluout),
               .zero    (zero));

endmodule

```

Since the original data path is not able to implement the LBU instruction, a module called `word_to_byte` is added to the data path. This module receive the data from the memory and also a `loadbyte` signal from the control signal. If the control signal gives a `loadbyte` signal of 1, the module will load one byte of the data from the memory instead of the whole 32 bit data. The position of the byte will be determined by the `whichbyte` signal which is decided from the least two significant bits of the `aluout` signal which is the memory address of the data.

4.1.7 Load Byte

 


Figure 7: ASM

```

module word_to_byte(input [31:0] a,
    input [1:0] whichbyte,
    input loadbyte,
    output reg [31:0] y);

always @(*)
begin
    if(loadbyte)
        case(whichbyte[1:0])
            2'b00: y <= {24'b0, a[7:0]};
            2'b01: y <= {24'b0, a[15:8]};
            2'b10: y <= {24'b0, a[23:16]};
            2'b11: y <= {24'b0, a[31:24]};
        endcase
    else

```

```

        y <= a[31:0];
    end

endmodule

```

This module determines whether a byte or a word is loaded from the memory. If a loadbyte signal is detected true, the module loads a byte, and the whichbyte signal decides which of the byte within the 32-bit data is loaded.

4.2 NOR

4.2.1 Assembly Language Code

```

# loads first operand
lui $s0, 0x0000
addiu $s0, $s0, 0x0f0f
# loads second operand
lui $s1, 0x0000
addiu $s1, $s1, 0x00ff
# the address of LED_R
lui $t0, 0x0000
addiu $t0, $t0, 0x2008
# 0x0F0F nor 0x00FF
nor $s2, $s0, $s1
# LED_R to display the result
sw $s2, 0x0000($t0)

```

4.2.2 ModelSim Result

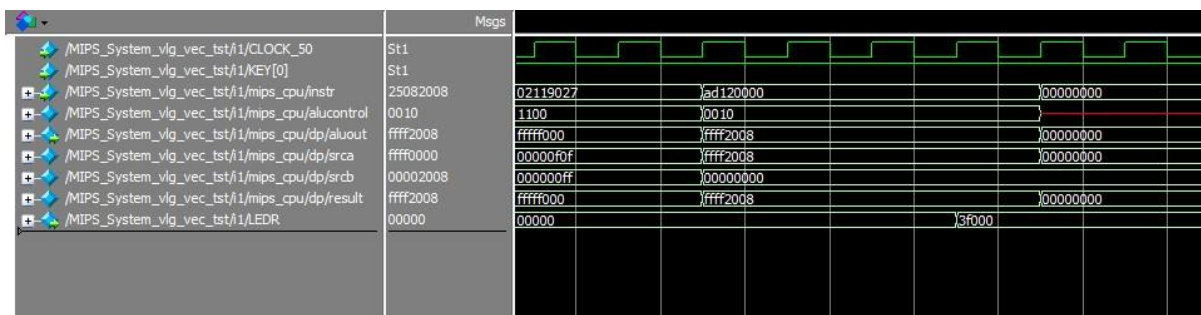


Figure 8: ModelSim Simulation Result

As shown in Figure 8, the simulation result shows that the function of the NOR instruction is working properly. It can be seen that for the clock cycle of the NOR instruction, the alucontrol signal is 1100. Meanwhile, the two inputs to the ALU is hexadecimal 0000 0F0F and 0000 00FF. Since

$$000\ 00F0F\ NOR\ 0000\ 00FF = FFFF\ F000$$

As the lower 18 bits is stored into the LEDR address, the result becomes 11 1111 0000 0000 0000, which is 3f000 as shown in the figure.

4.3 ANDI

4.3.1 Assembly Language Code

```
# loads first operand
lui $s0, 0x0000
addiu $s0, $s0, 0x0f0f
# the address of LED_R
lui $t0, 0xffff
addiu $t0, $t0, 0x2008
# 0x0F0F and 0x00FF
andi $s2, $s0, 0x00ff
# LED_R to display the result
sw $s2, 0x0000($t0)
```

4.3.2 ModelSim Result

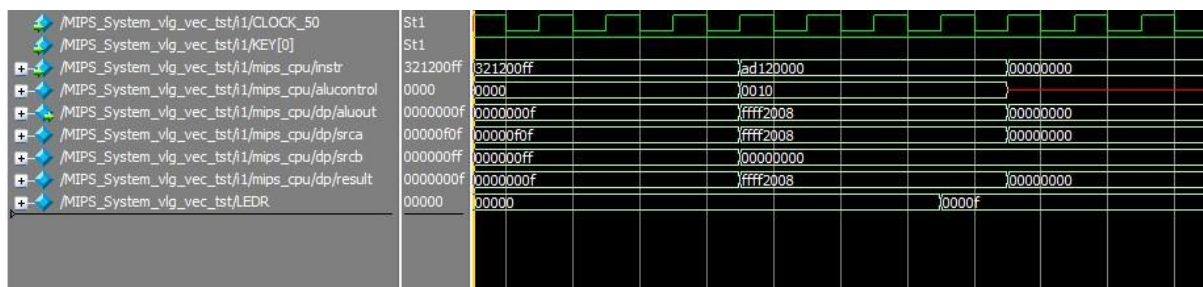


Figure 9: ModelSim Simulation Result

This instruction conducts an AND operation between 00000F0F and 000000FF. Since

$$0000\ 0F0F\ AND\ 0000\ 00FF = 0000\ 000F$$

Hence, the result shown on the LEDR is a 18 bits number which is 0000F in hexadecimal.

4.4 LBU

4.4.1 Assembly Language Code

```
# loads first operand
lui $s0, 0x0000
addiu $s0, $s0, 0x5500
# a temporary memory address
lui $t0, 0x0000
addiu $t0, $t0, 0x2000
# the address of LED_R
lui $t1, 0xffff
addiu $t1, $t1, 0x2008
```

```

# stores 0x0000 5500 to mem(0x0000 2000)
sw $s0, 0x0000($t0)
# loads the second byte(0x55) from mem(0x0000 2000)
lbu $s1, 0x0001($t0)
# stores 0x0055 to the memory of LED_R
sw $s1, 0x0000($t1)

```

4.4.2 Additional Pathways Diagram

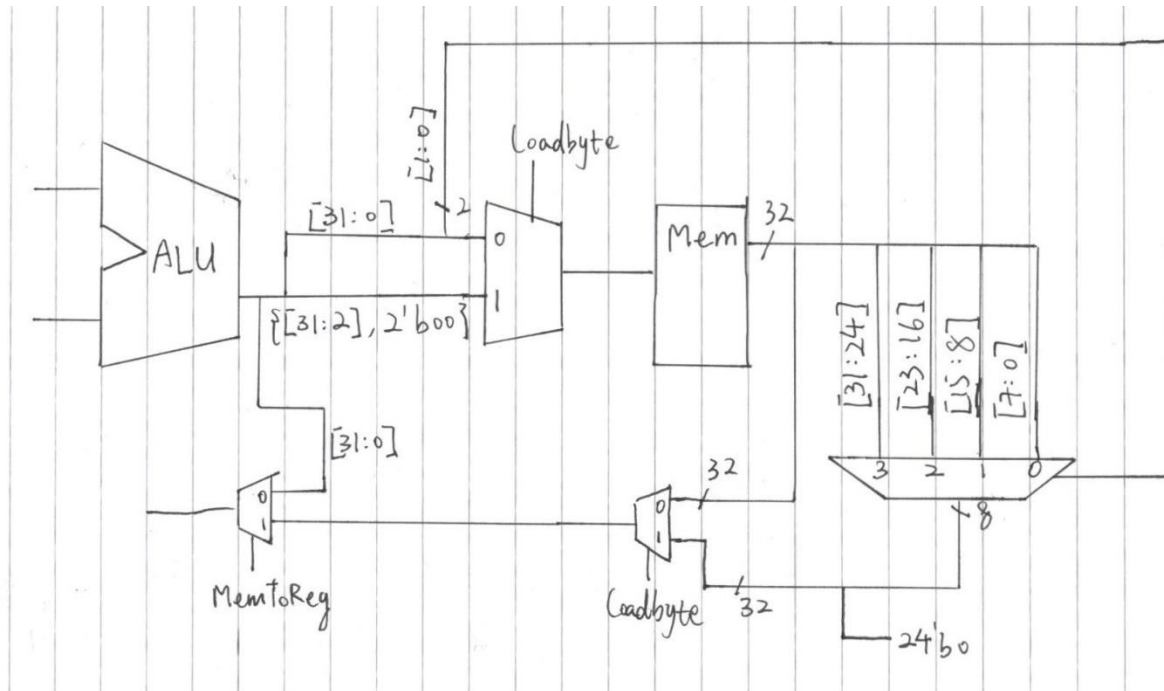


Figure 10: Block Diagram of Additional Pathways

As shown in the Block Diagram, one of the additional pathways is added between the ALU and the memory. Data will be separated as one full 32 bits data and one sliced 32 bits data with 2 bits of zeros replacing the least two significant bits. The original least two significant two bits is routed to the other additional mux to determine which byte of the data should be loaded. The loadbyte signal will determine whether the byte data is loaded to the register or rather a full 32 bit one.